



- The amount of total capacitance depends on the impedance range to be matched.
- The switched capacitors can be implemented either with a rotary switch, or with jumpers.
- For high or very low impedances, you may need more capacitance. Therefore you should provision for adding an external Cap on the back panel of the matchbox.
- For Symmetrical feedline, use an external 1:1 Guanella Balun.
  - Best is with 100 Ohm twisted pair or bifilar feedline.
  - Coax usually will work just as well, especially if the impedance to be matched is not too high. (KISS)



Balun Info: <http://www.dj0ip.de/balun-stuff/tuner-baluns/d-i-y-tuner-balun/>